



THE UNIVERSITY OF BRITISH COLUMBIA

Martin Alejo

#75296665

December 9, 2022

Mini Project 4

University of British Columbia

Electrical and Computer Engineering

ELEC 301

Instructor: Nicolas Jaeger

A handwritten signature in black ink, appearing to read 'Martin'.

Contents

List of Figures

List of Tables

1 Introduction

For this project, we will be using SPICE software to simulate active filters and oscillators.

2 Part A

For this part, we will be designing a 2nd order Butterworth low pass active filter using the UA741 operational amplifier.

Here is the circuit that we will be using for this part:



Figure 1: Second Order Butterworth Filter

The calculations to find the resistance R_1, R_2 and capacitance C , we will be using the formulas from the class notes [1].

3 Part B

4 Part C

5 References

1. ELEC 301 Class notes
2. Mini Project 4 Document
3. Standard Resistor and Capacitor Values (Canvas)
4. Circuit Maker SPICE Model