



THE UNIVERSITY OF BRITISH COLUMBIA

Martin Alejo

#75296665

December 9, 2022

Mini Project 4

University of British Columbia

Electrical and Computer Engineering

ELEC 301

Instructor: Nicolas Jaeger

A handwritten signature in black ink, appearing to read 'Martin'.

Contents

1	Introduction	1
2	Part A	1
2.0.1	Part 1	1
3	Part B	1
4	Part C	1
5	Appendix	1
6	References	1

List of Figures

1	Second Order Butterworth Filter	1
---	---	---

List of Tables

1 Introduction

For this project, we will be using SPICE software to simulate active filters and oscillators.

2 Part A

2.0.1 Part 1

For this part, we will be designing a 2nd order Butterworth low pass active filter using the UA741 operational amplifier. Here is the circuit that we will be using for this part:

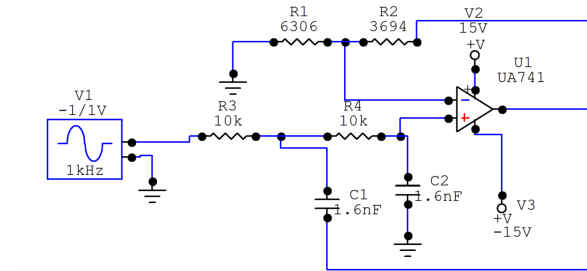


Figure 1: Second Order Butterworth Filter

The calculations to find the resistance R_1, R_2 and capacitance C , we will be using the formulas from the class notes [1]. The formulas can also be found from no. 1 in the Appendix.

3 Part B

4 Part C

5 Appendix

$$k = 3 - \sqrt{(2)} \quad (1)$$

(2)

6 References

1. ELEC 301 Class notes
2. Mini Project 4 Document
3. Standard Resistor and Capacitor Values (Canvas)
4. Circuit Maker SPICE Model